

Nama = Ian Feux Jonathan. S.

NRP = 05311940000008

Dept = Teknologi Informasi


1) An air conditioner connected to a 120 V rms ac line is equivalent to a  $12\ \Omega$  resistance and a  $1.30\ \Omega$  inductive reactance in series. calculate a) impedance of the air conditioner and b) The average rate which energy is supplied to the appliance.

Jawab =

$$\begin{aligned} a) \quad Z &= \sqrt{R^2 + (X_L - X_C)^2} \\ &= \sqrt{12^2 + (1.3 - 0)^2} \\ &= \sqrt{144 + 1.69} \\ &= 12.07\ \Omega \end{aligned}$$

$$\begin{aligned} b) \quad P_{rata} &= I_{rms}^2 R = \left[ \frac{\mathcal{E}_{rms}}{Z} \right]^2 R \\ P_{rata} &= \left( \frac{120}{12.07} \right)^2 \cdot 12 \\ &= 1.186 \times 10^3\text{ W} \end{aligned}$$

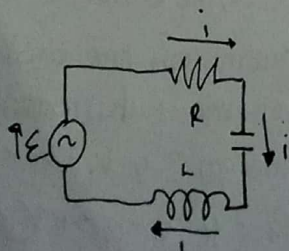2) In Fig. 31-7,  $R = 15.0\ \Omega$ ,  $C = 4.7\ \text{pF}$  dan  $L = 25.0\text{ mH}$ . The generator provides an emf with rms voltage 75.0 V and frequency 550 Hz. a) what is the rms current? what is the rms voltage across b) R, c) C, d) L e) C dan L together and f) R, C dan L together? At what average rate is energy dissipated by (g) R, h) C and (i) L?



a) rms current

$$\begin{aligned} I_{rms} &= \frac{\mathcal{E}_{rms}}{Z} = \frac{\mathcal{E}_{rms}}{\sqrt{R^2 + (2\pi fL - 1/2\pi fC)^2}} \\ &= \frac{75}{\sqrt{15^2 + (2\pi(550)(25\text{ mH}) - 1/2\pi(550)(4.7\text{ pF}))^2}} \\ &= 2.59\text{ A} \end{aligned}$$

$$\begin{aligned} b) \quad V_{ab} &= I_{rms} R \\ &= 2.59 \times 15 \\ &= 38.8\text{ V} \end{aligned}$$

$$\begin{aligned} c) \quad V_{bc} &= I_{rms} X_C = \frac{I_{rms}}{2\pi f C} \\ &= \frac{2.59}{2\pi \times 550 \times 4.7 \times 10^{-6}} \\ &\approx 159\text{ V} \end{aligned}$$

$$\begin{aligned} d) \quad V_{cd} &= I_{rms} X_L \\ &= I_{rms} \times 2\pi f L \\ &= 2.59 \times 2\pi \times 550 \times 25 \times 10^{-3} \\ &\approx 224\text{ V} \end{aligned}$$

$$\begin{aligned} e) \quad V_{bd} &= |V_{bc} - V_{cd}| \\ &= |159.5 - 223.7| = 64.2\text{ V} \end{aligned}$$

$$\begin{aligned} g) \quad P_R &= \frac{V_{ab}^2}{R} = \frac{(38.8)^2}{15} \\ &\approx 100\text{ W} \end{aligned}$$

$$h) \quad P_C = 0$$

$$i) \quad P_L = 0$$

3) In a series oscillating RLC circuit,  $R = 16.0\ \Omega$ ,  $C = 31.2\ \text{pF}$ ,  $L = 91.2\ \text{mH}$ , and  $\mathcal{E}_m = \mathcal{E}_m \sin \omega t$  with  $\mathcal{E}_m = 45.0\text{ V}$  and  $\omega = 3000\text{ rad/s}$ . For time  $t = 0.442\text{ ms}$  find a) the rate  $P_g$  at which energy is being supplied by the generator, b) the rate  $P_C$  at which the energy in the capacitor is changing, c) the rate  $P_L$  at which the energy in the inductor is changing, and d) the rate  $P_R$  at which energy is being dissipated in the resistor. e) is the sum of  $P_C$ ,  $P_L$ , and  $P_R$  greater than, less than or equal to  $P_g$ ?

Nama = Ian Felix Jonathan

NRP = 0531940000000

Dept = Teknologi Informasi

Jawab)

$$I = \frac{E_m}{Z} = \frac{E_m}{\sqrt{R^2 + (\omega L - \omega C)^2}}$$

$$I = \frac{45}{\sqrt{16^2 + \left(3000 \times 9,20 \times 10^{-3} - \frac{1}{3000 \times 31,2 \times 10^{-6}}\right)^2}}$$

$$\approx 1,93 \text{ A}$$

$$i(t) = I \sin(\omega t - \phi)$$

$$\begin{aligned}\phi &= \tan^{-1} \left[ \frac{X_L - X_C}{R} \right] = \tan^{-1} \left[ \frac{\omega L - 1/\omega C}{R} \right] \\ &= \tan^{-1} \left[ \frac{(3000)(9,2 \cdot 10^{-3}) - \frac{1}{(3000)(16 \times 31,2 \times 10^{-6})}}{16} \right] \\ &= 46,5^\circ\end{aligned}$$

$$\begin{aligned}q) P_g &= i(t)E(t) = I \sin(\omega t - \phi) E_m \sin \omega t \\ &= 1,93 \times 45 \sin(3000 \times 0,442) \sin(3000 \times 0,442 - 46,5) \\ &\approx 41,4 \text{ W}\end{aligned}$$

$$\begin{aligned}b) V_C &= V_C \sin(\omega t - \phi - \pi/2) = -V_C \cos(\omega t - \phi) \\ \text{Ketika } V_C &= 1/\omega C\end{aligned}$$

$$\begin{aligned}P_C &= \frac{d}{dt} \left[ \frac{q^2}{2C} \right] = I \frac{q}{C} = IV_C \\ &= -I \sin(\omega t - \phi) \left( \frac{1}{\omega C} \right) \cos(\omega t - \phi) \\ &= -\frac{I^2}{2\omega C} \sin(2(\omega t - \phi)) \\ &= \frac{(1,93)^2}{2 \times 3000 \times 31,2 \times 10^{-6}} \sin(2(3000 \times 0,442) - 2(46,5)) \\ &\approx -17,0 \text{ W}\end{aligned}$$

$$\begin{aligned}c) P_L &= \frac{d}{dt} \left( \frac{1}{2} Li^2 \right) = LI \sin(\omega t - \phi) \frac{d}{dt} [I \sin(\omega t - \phi)] \\ &= Li \frac{di}{dt} = \frac{1}{2} \omega L I^2 \sin(2(\omega t - \phi))\end{aligned}$$

$$\begin{aligned}P_L &= \frac{1}{2} (3000 \times 1,93^2 \times 9,2 \times 10^{-3} \sin(2(3000 \times 0,442) - 46,5)) \\ &\approx 41,1 \text{ W}\end{aligned}$$

$$\begin{aligned}d) P_R &= I^2 R \\ &= I^2 R \sin^2(\omega t - \phi) \\ &= 1,93^2 \times 16 \sin^2(3000 \times 0,442 - 46,5) \\ &\approx 14,4 \text{ W}\end{aligned}$$

$$\begin{aligned}e) P_L + P_R + P_C &= 41,1 - 17 + 14,4 = 41,5 \text{ W} \\ \text{karena } P_g &\approx 41,4 \\ \text{maka mereka memiliki nilai yang sama}\end{aligned}$$

4) A generator supplies 100V to a transformer's primary coil, which has 50 turns. If the secondary coil has 500 turns, what is the secondary voltage?

Jawab =

$$\frac{V_s}{V_p} = \frac{N_s}{N_p}$$

$$V_s = \frac{N_s}{N_p} V_p = \frac{500}{50} \cdot 100 = 1000 \text{ V}$$

5) An ac generator provides emf to a resistive load in a remote factory over a two-cable transmission line. At the factory a step-down transformer reduces the voltage from its (rms) transmission value  $V_t$  to a much lower value that is safe and convenient for use in the factory. The transmission line resistance is  $0,30 \Omega/\text{cable}$ , and the power generator is  $250 \text{ kW}$ . If  $V_f = 80 \text{ kV}$  what are (a) the voltage decrease  $\Delta V$  along the transmission line and (b) the rate  $P_d$  at which energy is dissipated in the line as thermal energy? If  $V_t = 80 \text{ kV}$  what are (c)  $\Delta V$  and (d)  $P_d$ ? If  $V_t = 0,8 \text{ kV}$  what are (e)  $\Delta V$  and (f)  $P_d$ ?



Nama: Ian Feux Jonathan S

NRP: 05311940000008

Dept: Teknologi Informasi

a)  $\Delta V = I_{rms} \cdot R$

$$= \frac{P}{V_b} \cdot R$$

$$= \frac{250 \times 10^3}{80 \times 10^3} \cdot 0,30 = 119 \text{ V}$$

b)  $P_d = I_{rms}^2 R = (31,25)^2 (0,30) = 5,9 \text{ W}$

c)  $I_{rms} = \frac{250 \times 10^3}{8 \times 10^3}$   
 $= 31,25$

$$\Delta V = (31,25)(0,60) = 19 \text{ V}$$

d)  $P_d = (31,25)^2 (0,60) = 5,9 \times 10^2 \text{ W}$

e)  $I_{rms} = 250 \times 10^3 \left( \frac{1}{0,18 \times 10^3} \right) = 312,5 \text{ A}$

$$\Delta V = (312,5)(0,60) = 119 \times 10^2 \text{ V}$$

f)  $P_d = (312,5)^2 (0,60) = 5,9 \times 10^4 \text{ W}$